

# **MIPS ALU & GPR File**

**[GPR File - General Purpose Register File]**

# MIPS instruction set


R-type

add Rd, Rs, Rt      # Rd=Rs+Rt  
 sub Rd, Rs, Rt      # Rd=Rs-Rt  
 and Rd, Rs, Rt      # Rd=Rs AND Rt  
 or Rd, Rs, Rt        # Rd=Rs OR Rt  
 xor Rd, Rs, Rt      # Rd=Rs XOR Rt  
 slt Rd, Rs, Rt      # if Rs<Rt Rd=1 else Rd=0  
 jr Rs                # PC=Rs (note that Rd=0)



I-type

 addi Rt, Rs, imm    # Rt=Rs+ sext(imm)  
 lw Rt, imm(Rs)      # Rt=M[Rs + sext(imm)]  
 sw Rt, imm(Rs)      # M[Rs + sext(imm)]=Rt  
 beq Rs, Rt, label    # if Rs==Rt, PC=PC+4+ sext(imm)\*4  
                           # else            PC=PC+4  
 bne Rs, Rt, label    # same as beq with cond of Rs≠Rt  
 ori Rt, Rs, imm      # Rt=Rs OR imm (no sext)  
 lui Rt, imm          # Rt= imm<<16 (no sext)




j-type

j imm                # PC= imm\*4 (no sext)  
 jal imm              # PC= imm\*4, \$31=PC+4 (no sext)




# The pipelined MIPS

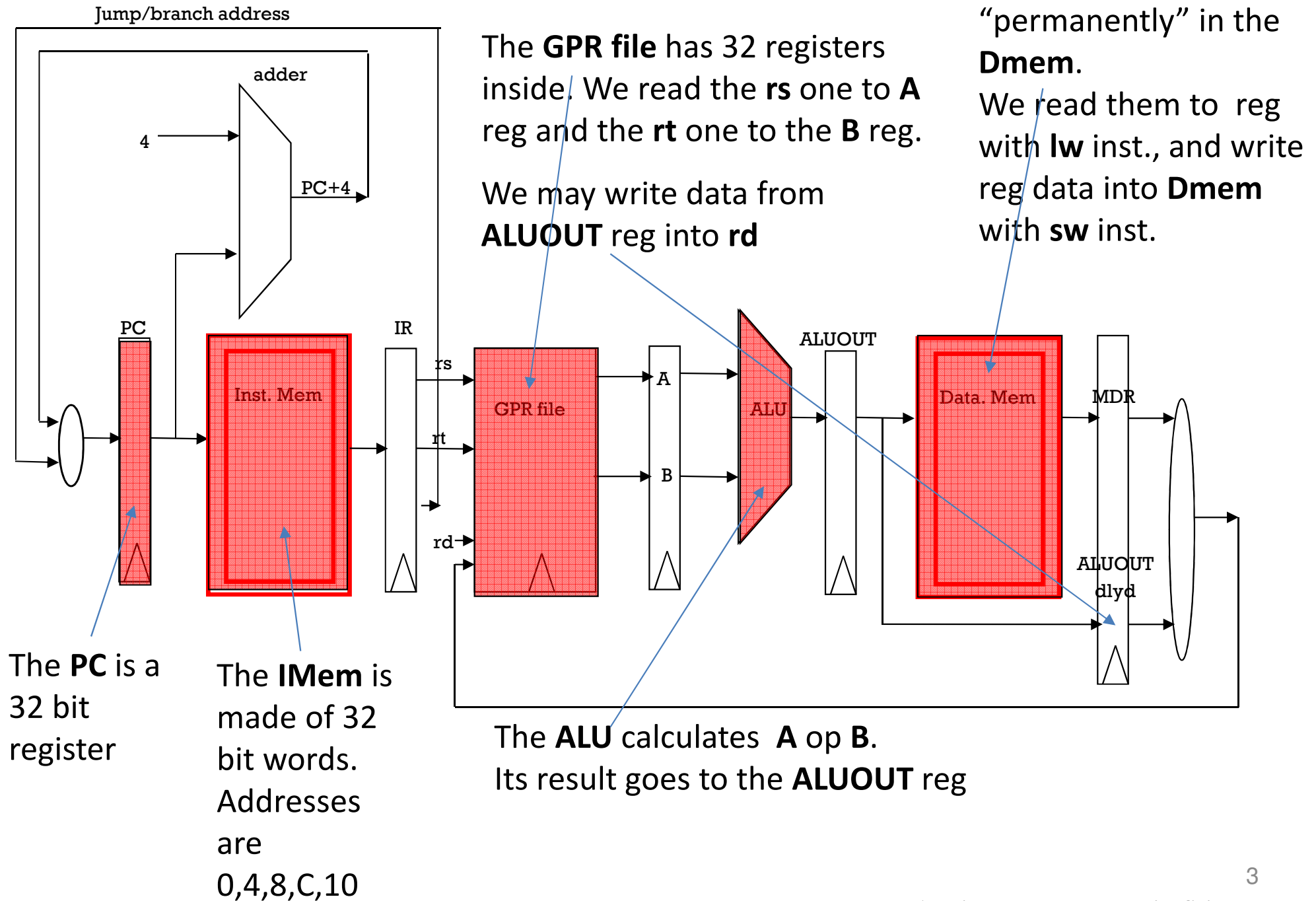

# **Rtype instructions**

# Performing Rtype inst.

 


The diagram illustrates the internal structure and data flow of a processor, likely a MIPS architecture, showing the interaction between various components:

- PC (Program Counter):** Holds the current instruction address. It is connected to the **Inst. Mem.** and the **adder**.
- Inst. Mem. (Instruction Memory):** Provides instructions to the **IR** based on the address from the **PC**.
- IR (Instruction Register):** Holds the current instruction. It provides fields **rs**, **rt**, and **rd** to the **GPR file**.
- GPR file (General Purpose Register File):** Provides data from registers **A** and **B** to the **ALU**. It also receives the **rd** field from the **IR** to write back to a register.
- ALU (Arithmetic Logic Unit):** Performs operations on data from registers **A** and **B** based on the operation code from the **IR**. It outputs to **ALUOUT**.
- ALUOUT:** The output of the ALU, which is connected to the **Data. Mem.** and the **MDR**.
- Data. Mem. (Data Memory):** Provides data to the **MDR** based on the address from the **ALUOUT**.
- MDR (Memory Data Register):** Holds data from the **Data. Mem.** and provides it to the **ALUOUT dlyd**.
- ALUOUT dlyd:** A delayed version of the **ALUOUT**, which is connected back to the **PC** via a multiplexer.
- adder:** Adds 4 to the **PC** value to calculate **PC+4**, which is used for sequential instruction fetching.
- Jump/branch address:** A multiplexer selects between the original **PC** value and the **ALUOUT dlyd** to determine the next **PC** value.

```
IR = Imem[PC]
PC = PC+4
```

# Performing Rtype inst.

 


**ID – Inst. Decode**

**A = rs , B = rt**

(& decode  
control signals)

# Performing Rtype inst.

 


**EX– Execute**

**ALUOUT = A op B**




# Performing Rtype inst.

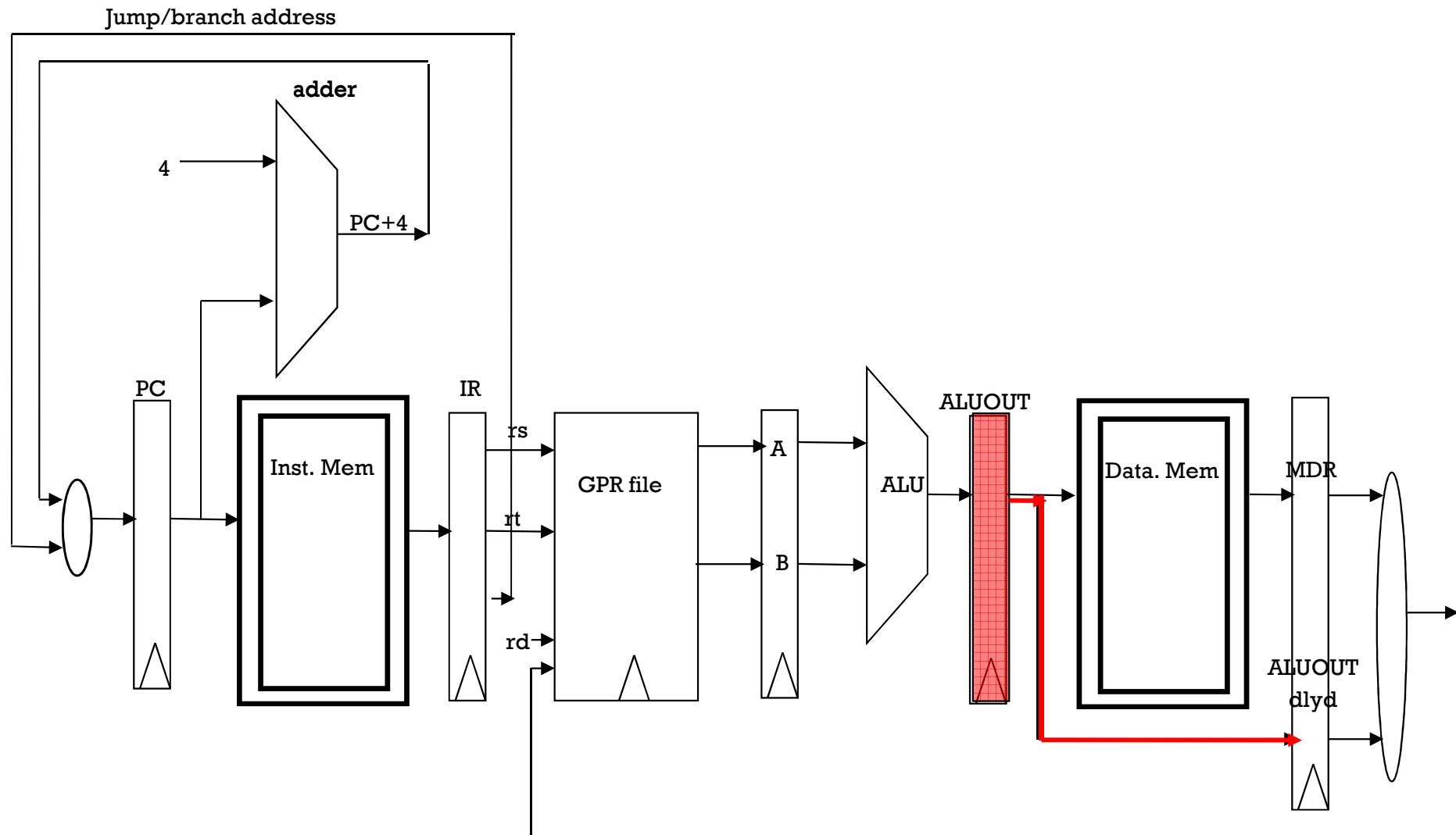

**MEM – Memory**

**In Rtype – wait 1 ck**

# Performing Rtype inst.

 


**WB – write back**

**Rd = ALUOUT**

# The ALU

# Performing Rtype inst.

 

**EX- Execute**


**ALUOUT = A op B**

# MIPS ALU


```
-- MIPS ALU
process(ALU_A_in, ALU_B_in, ALU_cmd, sign_of_sub)
begin
  case ALU_cmd is
    when b"000" => ALU_output <= ALU_A_in and ALU_B_in;-- AND
    when b"001" => ALU_output <= ALU_A_in or ALU_B_in; -- OR
    when b"010" => ALU_output <= ALU_A_in + ALU_B_in; -- ADD
    when b"011" => ALU_output <= ALU_A_in xor ALU_B_in; -- XOR
    when b"100" => ALU_output <= not(ALU_A_in and ALU_B_in); -- ???
    when b"101" => ALU_output <= not(ALU_A_in or ALU_B_in); --???
    when b"110" => ALU_output <= ALU_A_in - ALU_B_in; -- SUB
    when others => ALU_output <= x"0000000" & b"000" & sign_of_sub;-- SLT
  end case;
end process;
```

# Pipelined operation

# Performing Rtype inst.

 

## Performing Rtype inst.

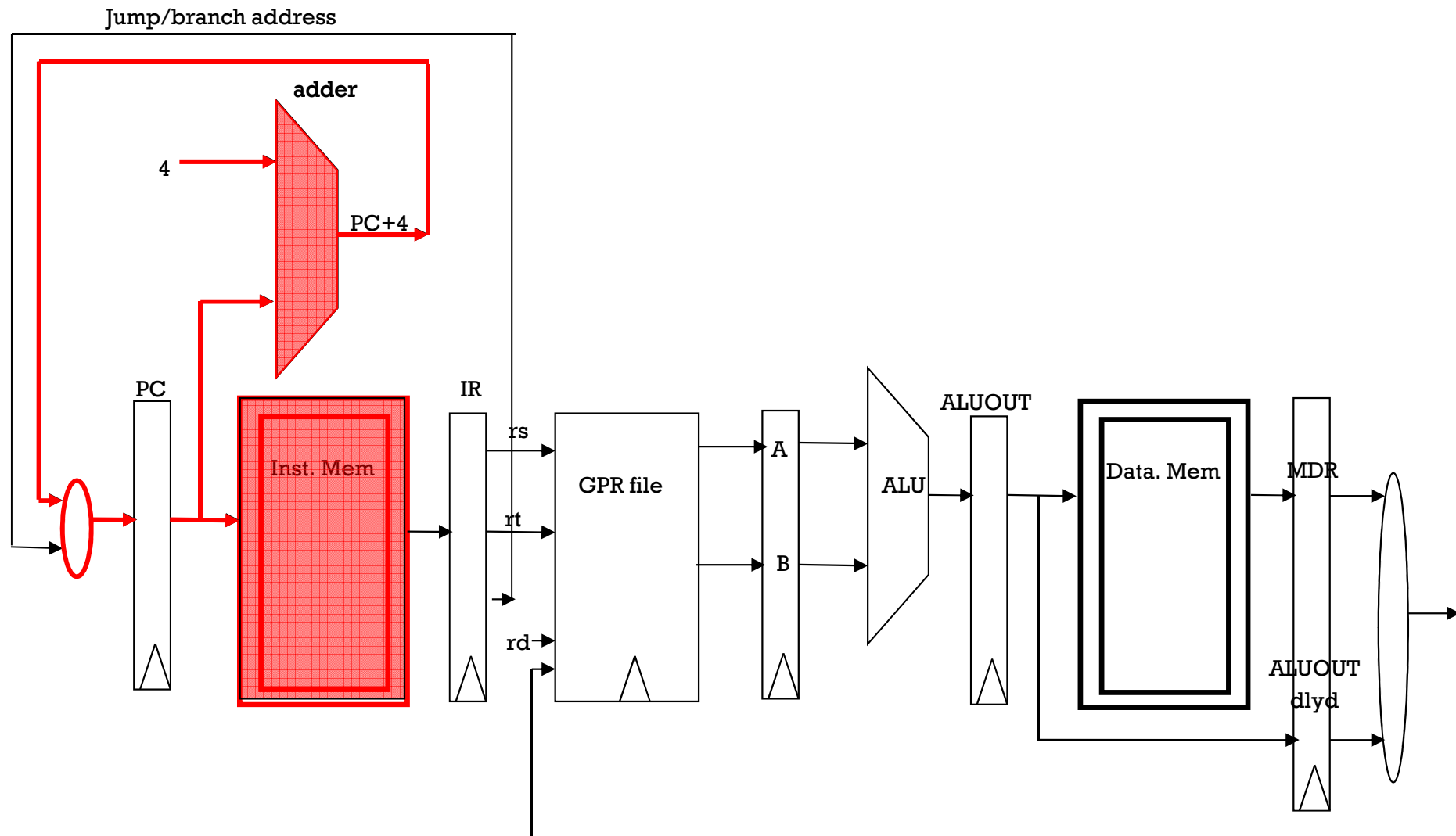


## IF – Inst. Fetch

**IR = Imem[PC]**

**PC = PC+4**



# Performing Rtype inst.

 

**IF – Inst. Fetch**


**IR = Imem[PC]  
PC = PC+4**

**ID – Inst. Decode**

**A = rs , B = rt**

(& decode  
control signals)

# Performing Rtype inst.

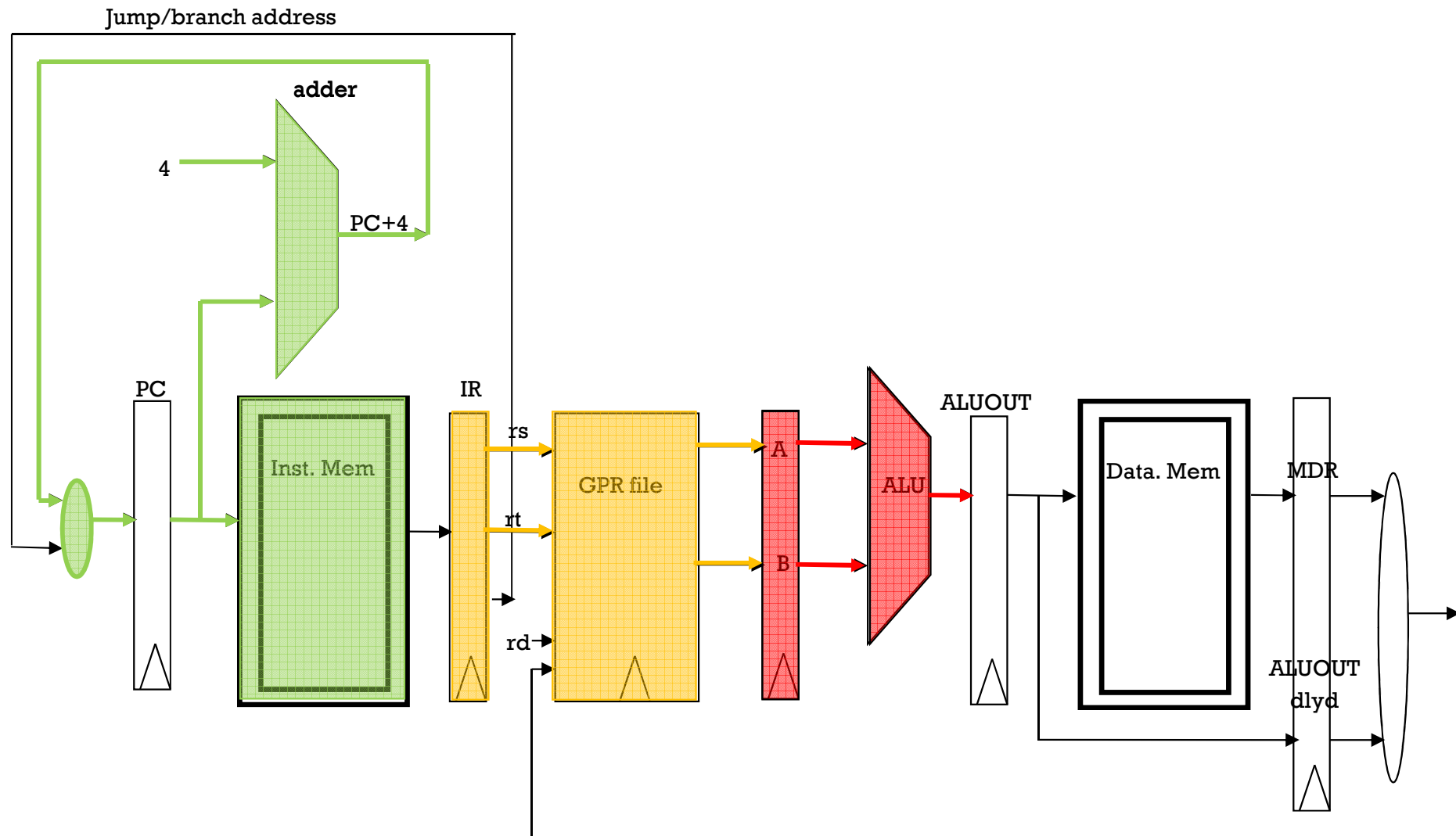

**IF – Inst. Fetch**

**IR = Imem[PC]  
PC = PC+4**


**ID – Inst. Dec.**  
**A = rs , B = rt**

(& decode  
control signals)

**EX– Execute**

**ALUOUT = A op B**

# Performing Rtype inst.

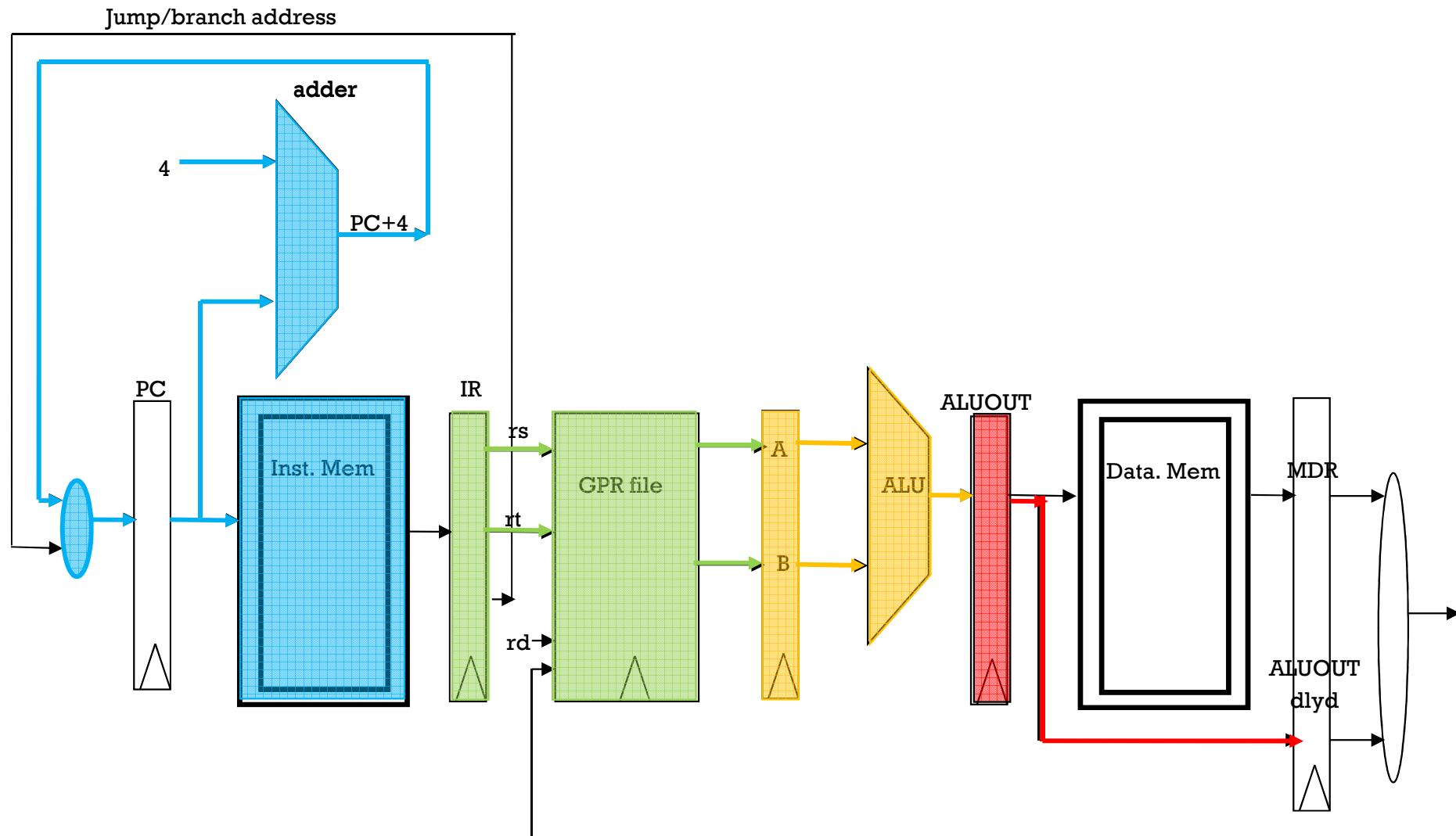

**IF – Inst. Fetch**

**IR = Imem[PC]  
PC = PC+4**

**ID – Inst. Dec.**

**A = rs , B = rt**

(& decode  
control signals)


**EX– Execute**

**ALUOUT = A op B**

**MEM**


**In Rtype –  
wait 1 ck**

# Performing Rtype inst.

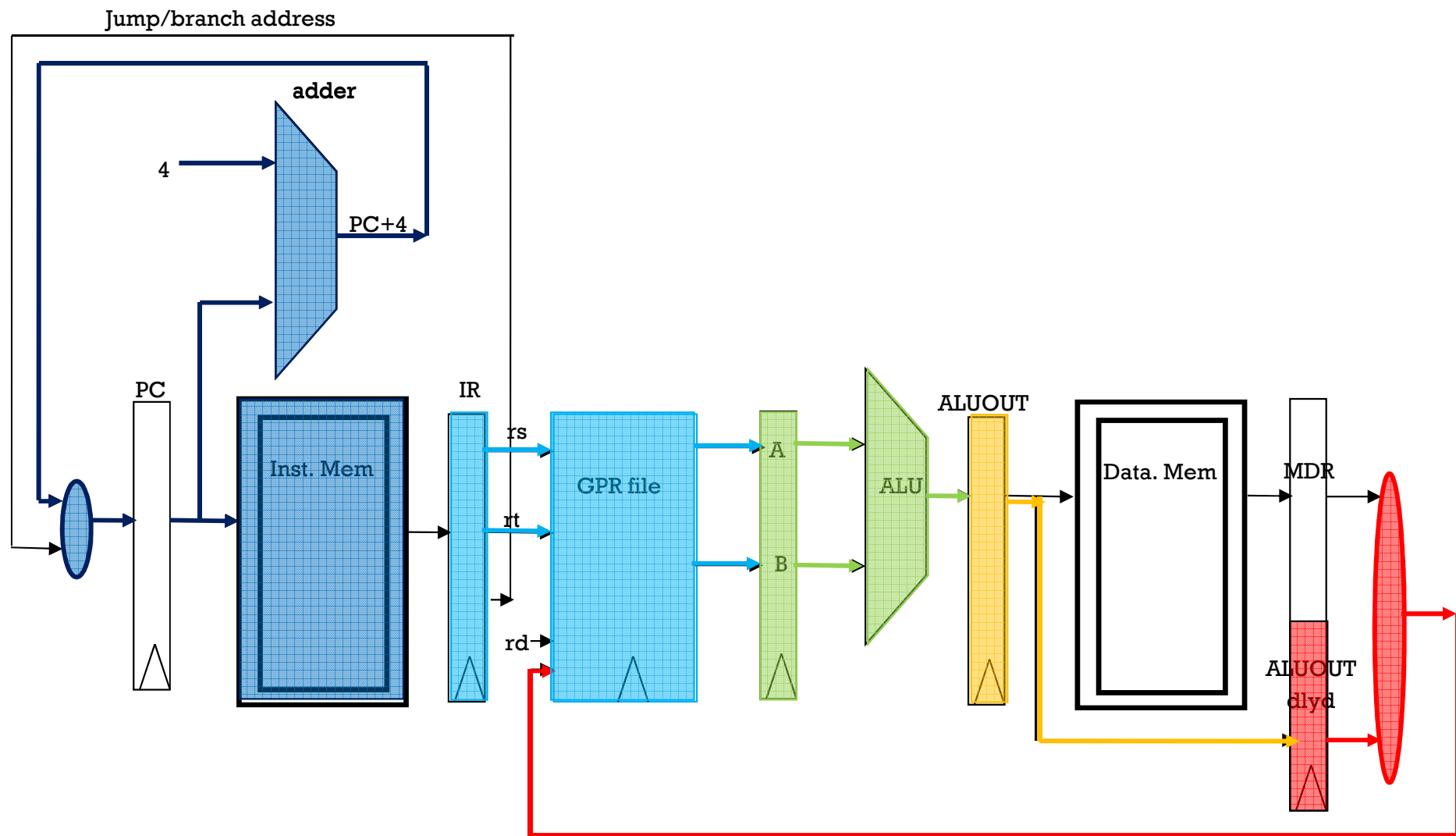


IF – Inst. Fetch	ID – Inst. Dec. A = rs , B = rt (& decode control signals)	EX– Execute ALUOUT = A op B	MEM In Rtype – wait 1 ck	WB – write back Rd = ALUOUT
IR = Imem[PC] PC = PC+4				

# Performing Rtype inst.

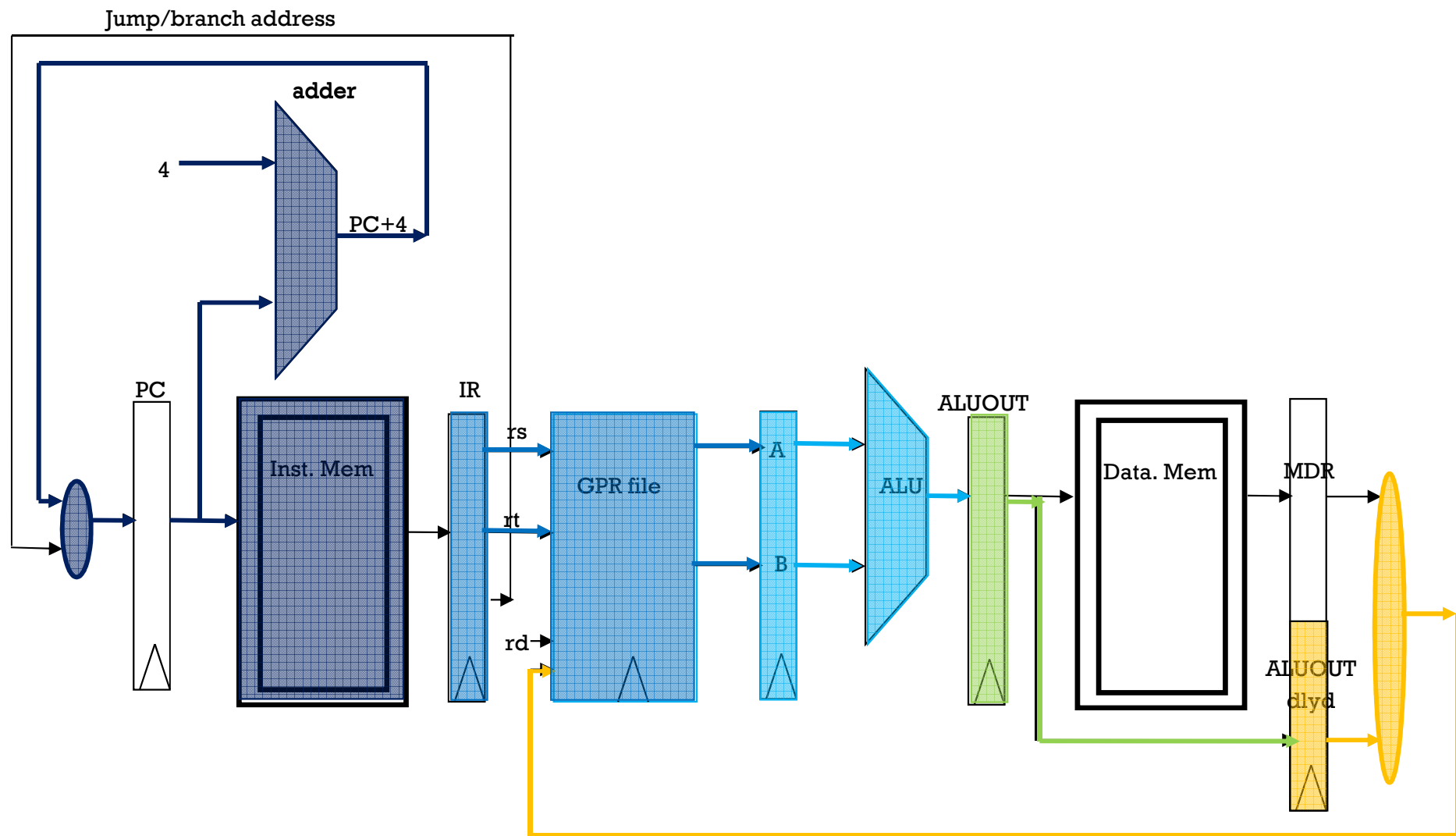

IF – Inst. Fetch	ID – Inst. Dec. A = rs , B = rt ( & decode control signals)	EX– Execute ALUOUT = A op B	MEM In Rtype – wait 1 ck	WB – write back Rd = ALUOUT
------------------	---	--------------------------------	-----------------------------	--------------------------------

# Performing Rtype inst.

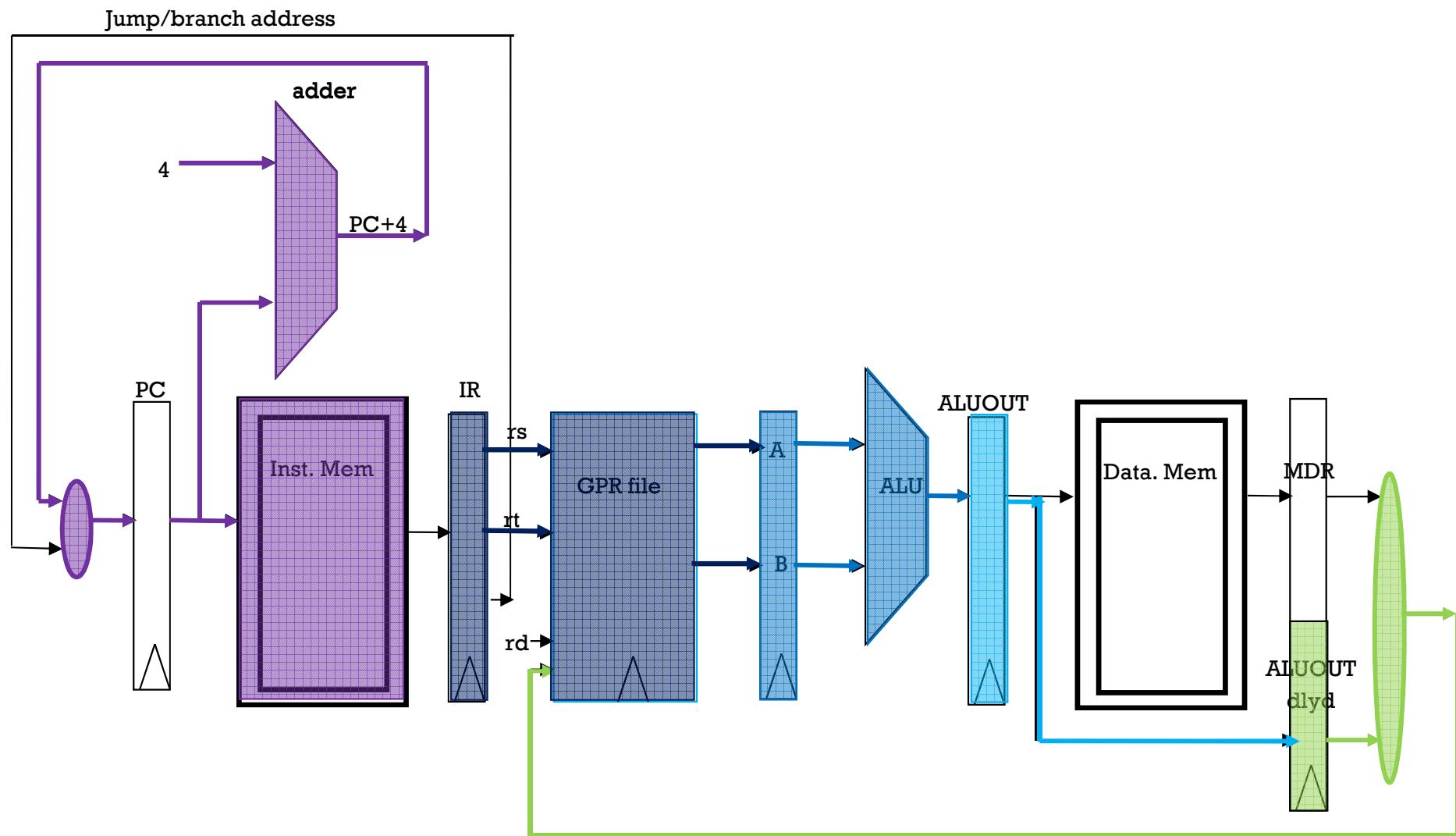

**IF – Inst. Fetch**

**IR = Imem[PC]  
PC = PC+4**

**ID – Inst. Dec.**

**A = rs , B = rt**  
( & decode  
control signals)

**EX– Execute**

**ALUOUT = A op B**


**MEM**

**In Rtype –  
wait 1 ck**

**WB – write back**

**Rd = ALUOUT**

# Performing Rtype inst.

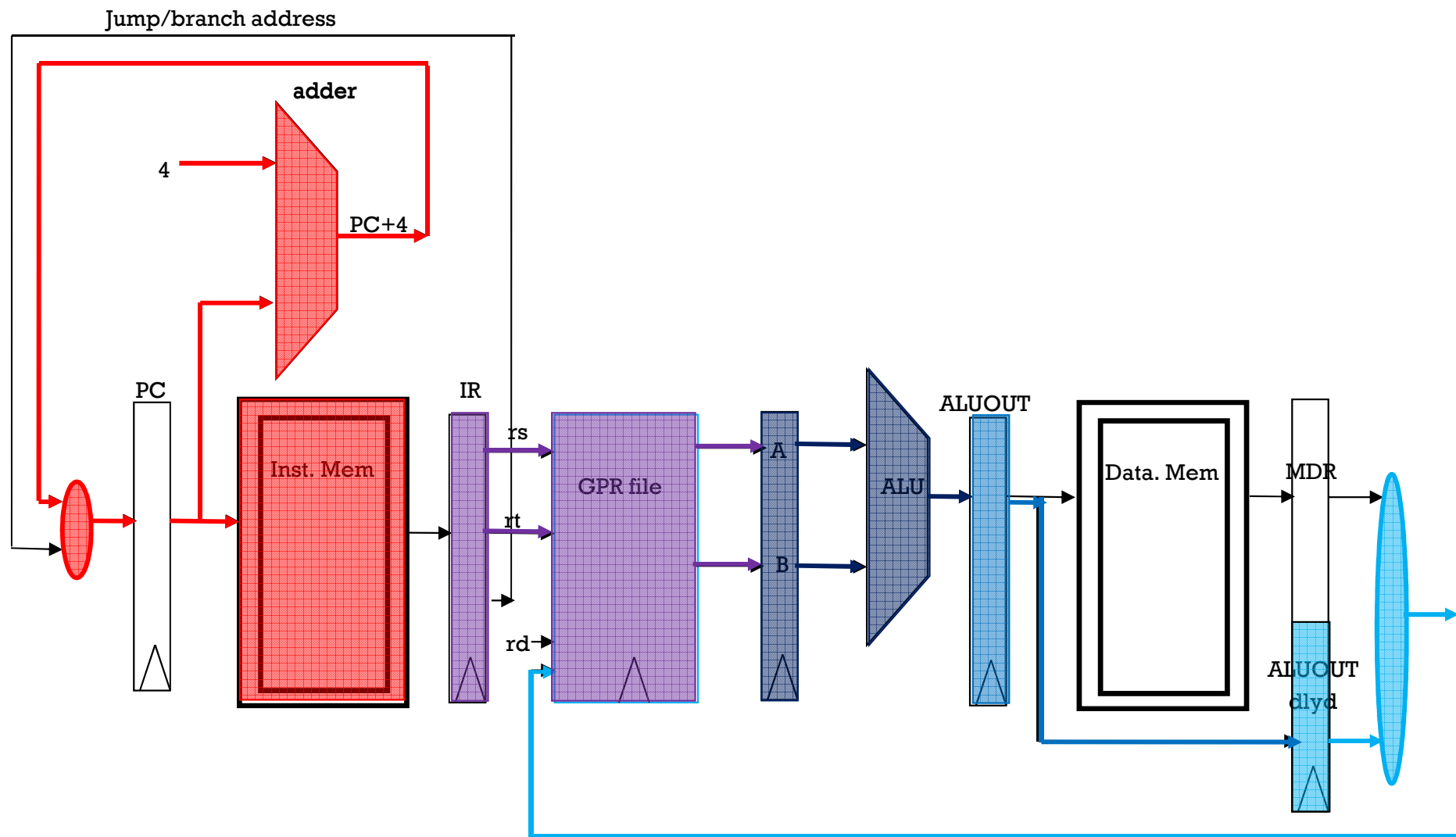

**IF – Inst. Fetch**

**IR = Imem[PC]**

**PC = PC+4**

**ID – Inst. Dec.**

**A = rs , B = rt**

(& decode control signals)

**EX– Execute**

**ALUOUT = A op B**


**MEM**

**In Rtype – wait 1 ck**

**WB – write back**

**Rd = ALUOUT**

# Performing Rtype inst.

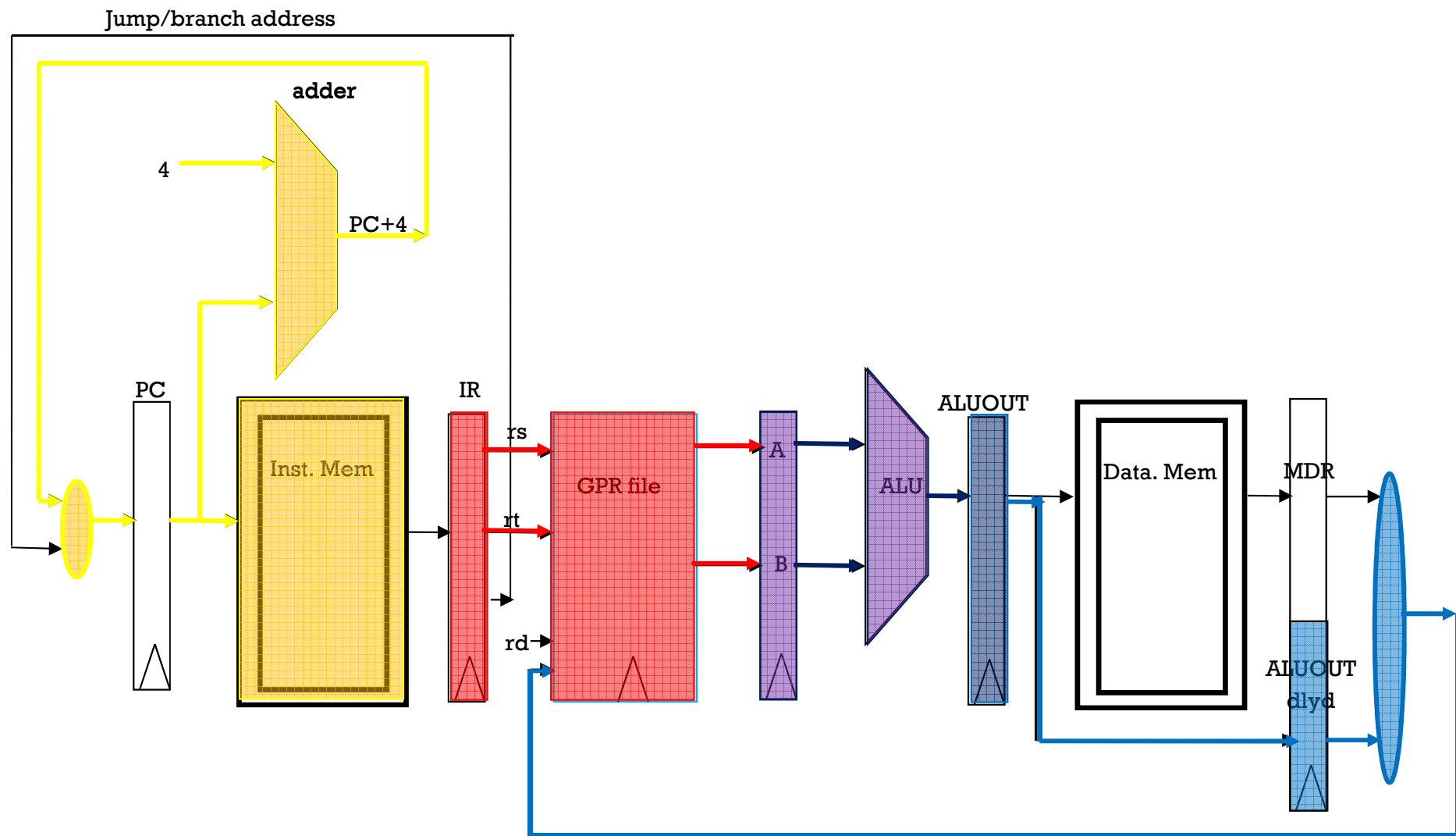

**IF – Inst. Fetch**

**IR = Imem[PC]  
PC = PC+4**

**ID – Inst. Dec.**

**A = rs , B = rt**

(& decode  
control signals)

**EX– Execute**

**ALUOUT = A op B**

**MEM**


**In Rtype –  
wait 1 ck**

**WB – write back**

**Rd = ALUOUT**



# Performing Rtype inst.

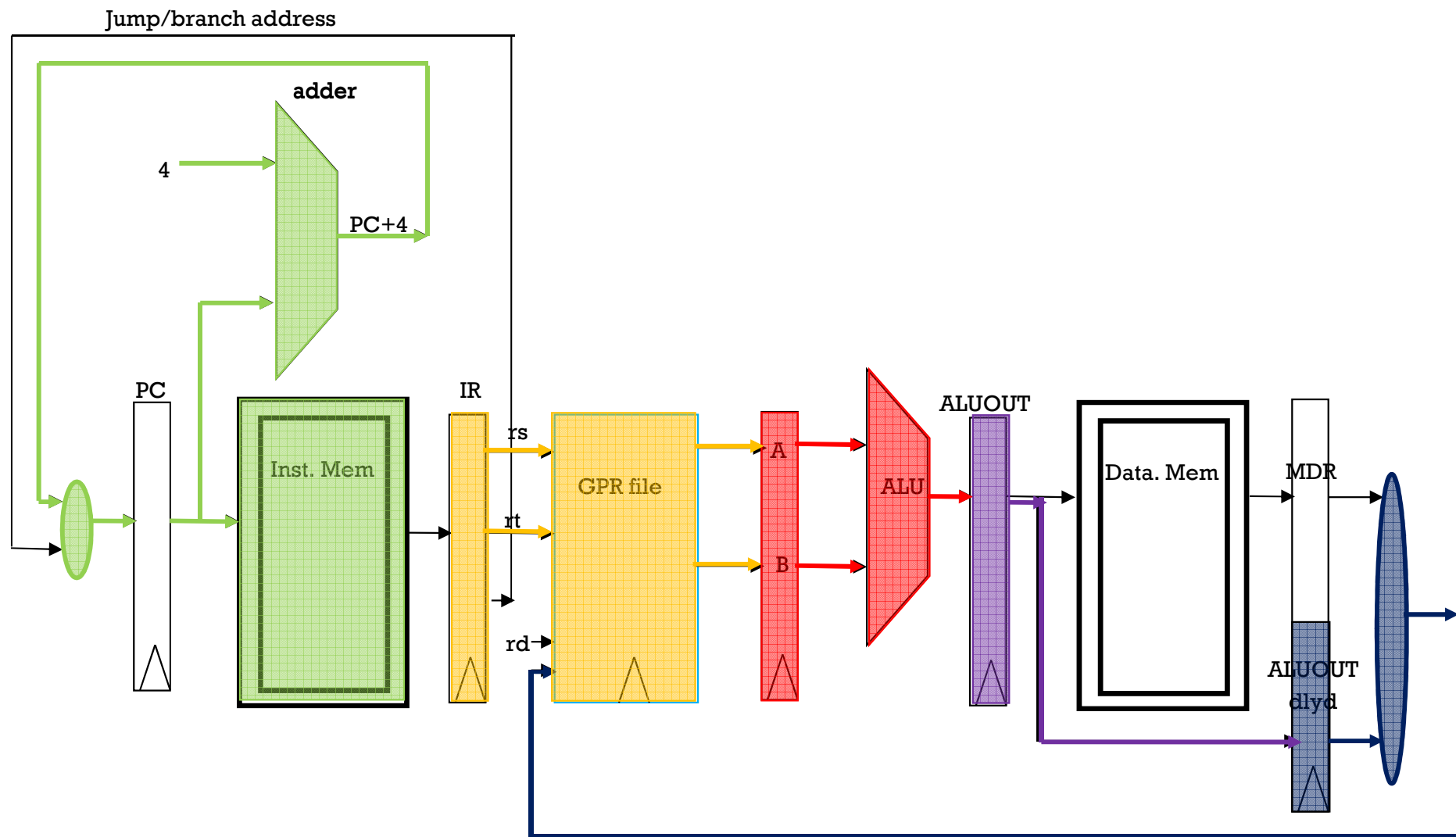

**IF – Inst. Fetch**

**IR = Imem[PC]  
PC = PC+4**

**ID – Inst. Dec.**

**A = rs , B = rt**

(& decode  
control signals)

**EX– Execute**

**ALUOUT = A op B**


**MEM**

**In Rtype –  
wait 1 ck**

**WB – write back**

**Rd = ALUOUT**

# Performing Rtype inst.

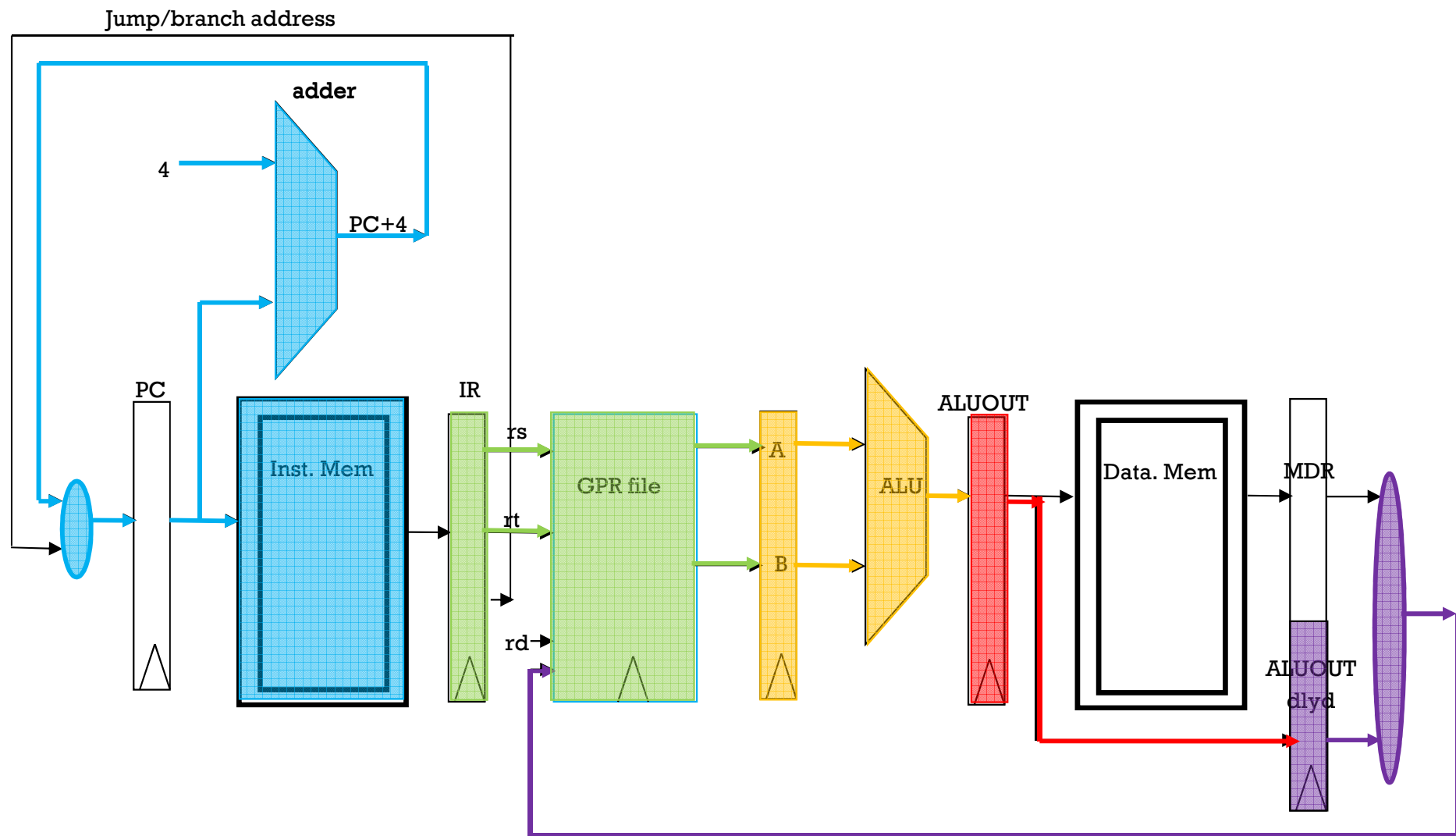

**IF – Inst. Fetch**

**IR = Imem[PC]  
PC = PC+4**


**ID – Inst. Dec.**  
**A = rs , B = rt**  
(& decode control signals)

**EX– Execute**  
**ALUOUT = A op B**

**MEM**  
**In Rtype – wait 1 ck**

**WB – write back**  
**Rd = ALUOUT**


# Performing Rtype inst.

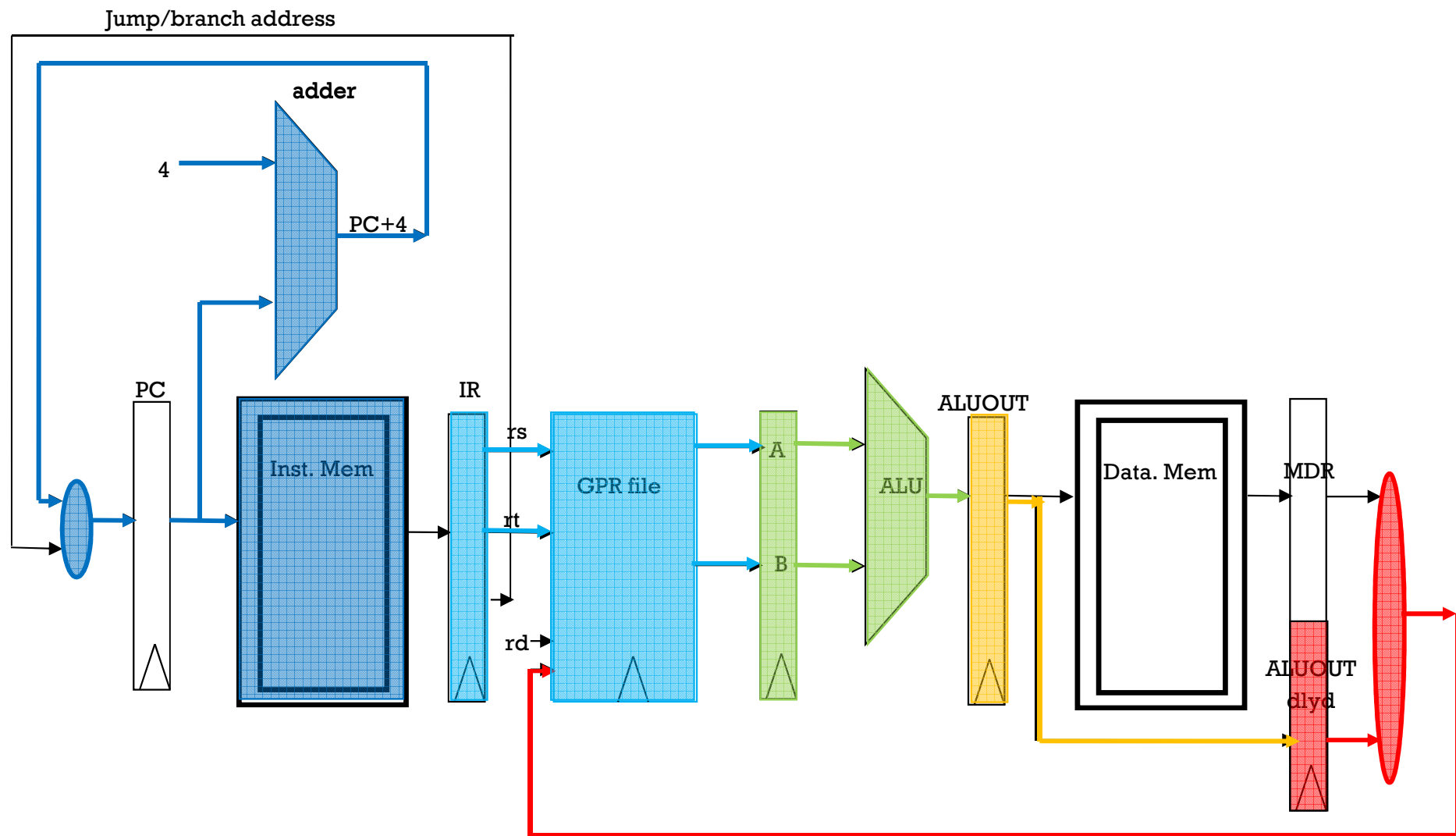


<b>IF – Inst. Fetch</b>  <b>IR = Imem[PC]</b> <b>PC = PC+4</b>	<b>ID – Inst. Dec.</b> <b>A = rs , B = rt</b> (& decode control signals)	<b>EX– Execute</b> <b>ALUOUT = A op B</b>	<b>MEM</b> <b>In Rtype – wait 1 ck</b>	<b>WB – write back</b> <b>Rd = ALUOUT</b>
---	--	--	---	--

# The GPR File


# Functional diagram

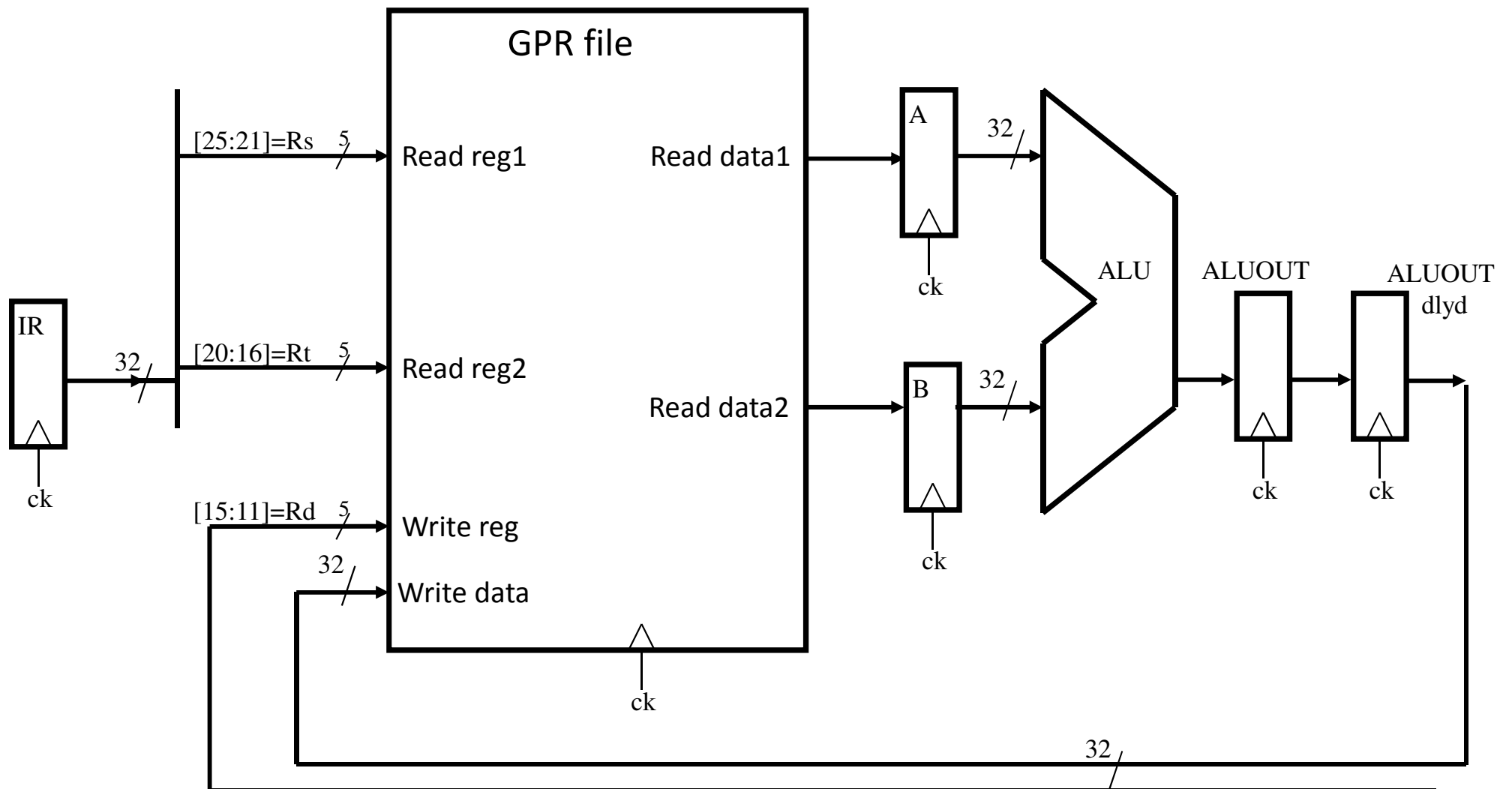

# Functional diagram

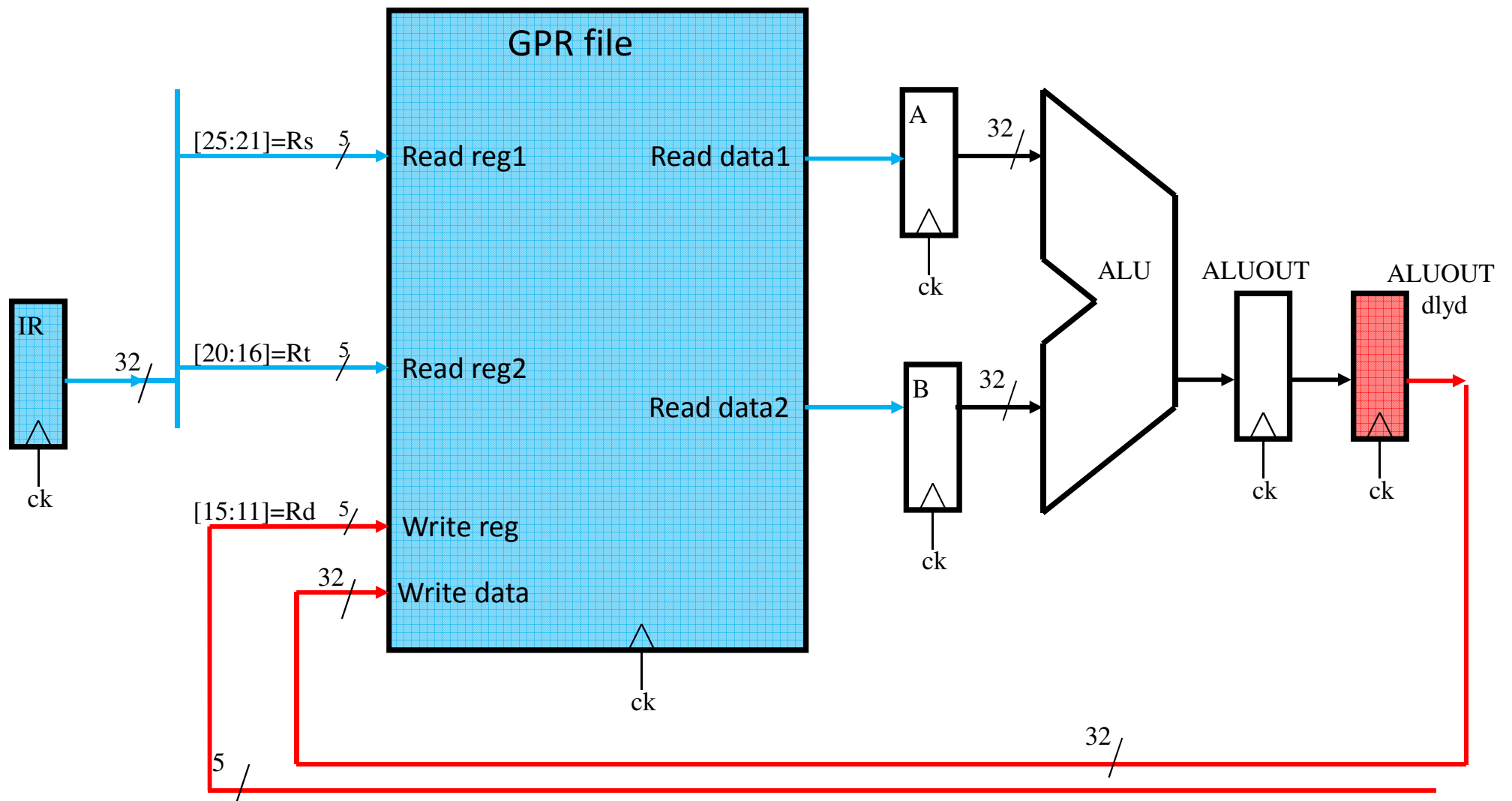

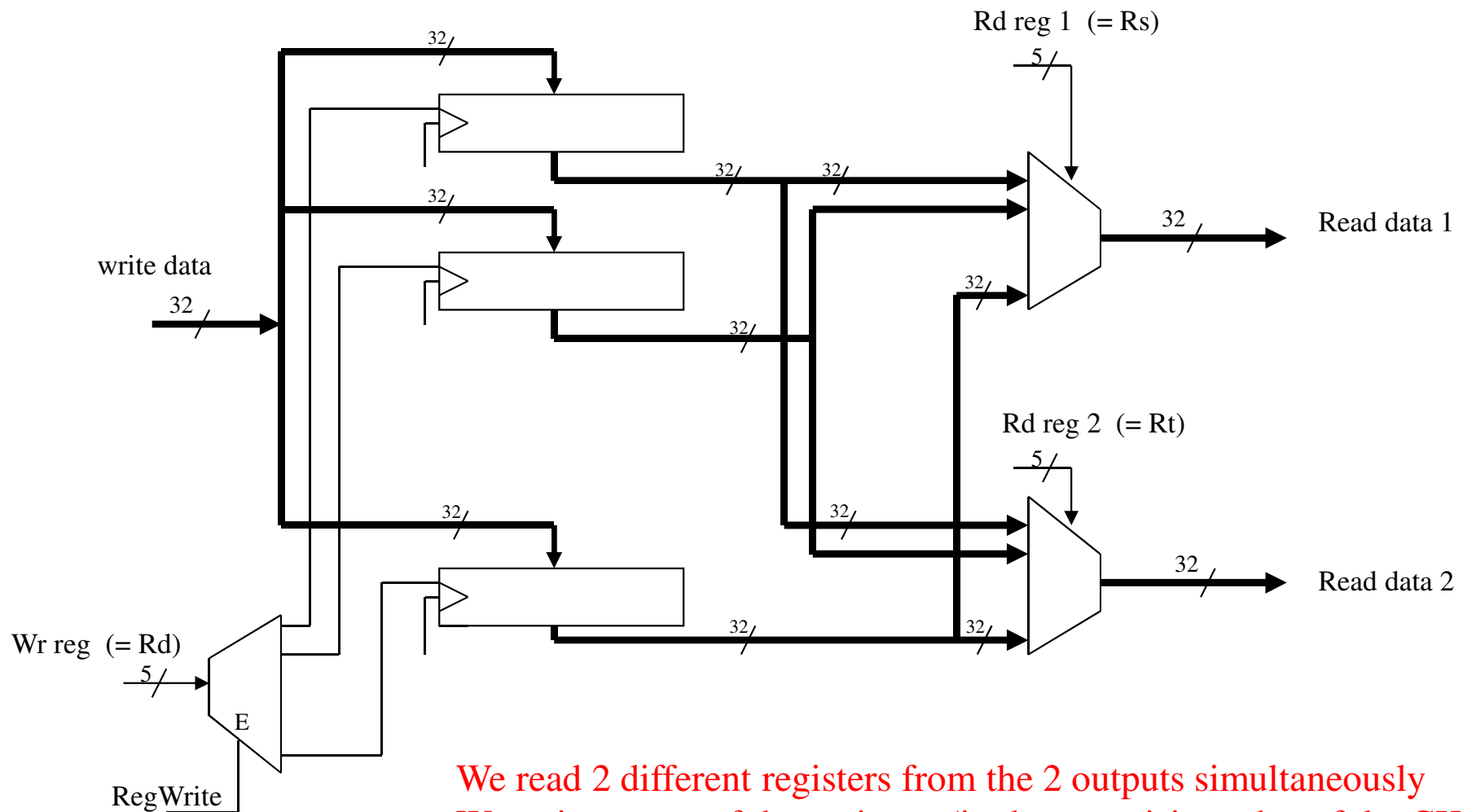
## One possible structure of the Register File




We read 2 different registers from the 2 outputs simultaneously  
We write to one of the registers (in the next rising edge of the CK).
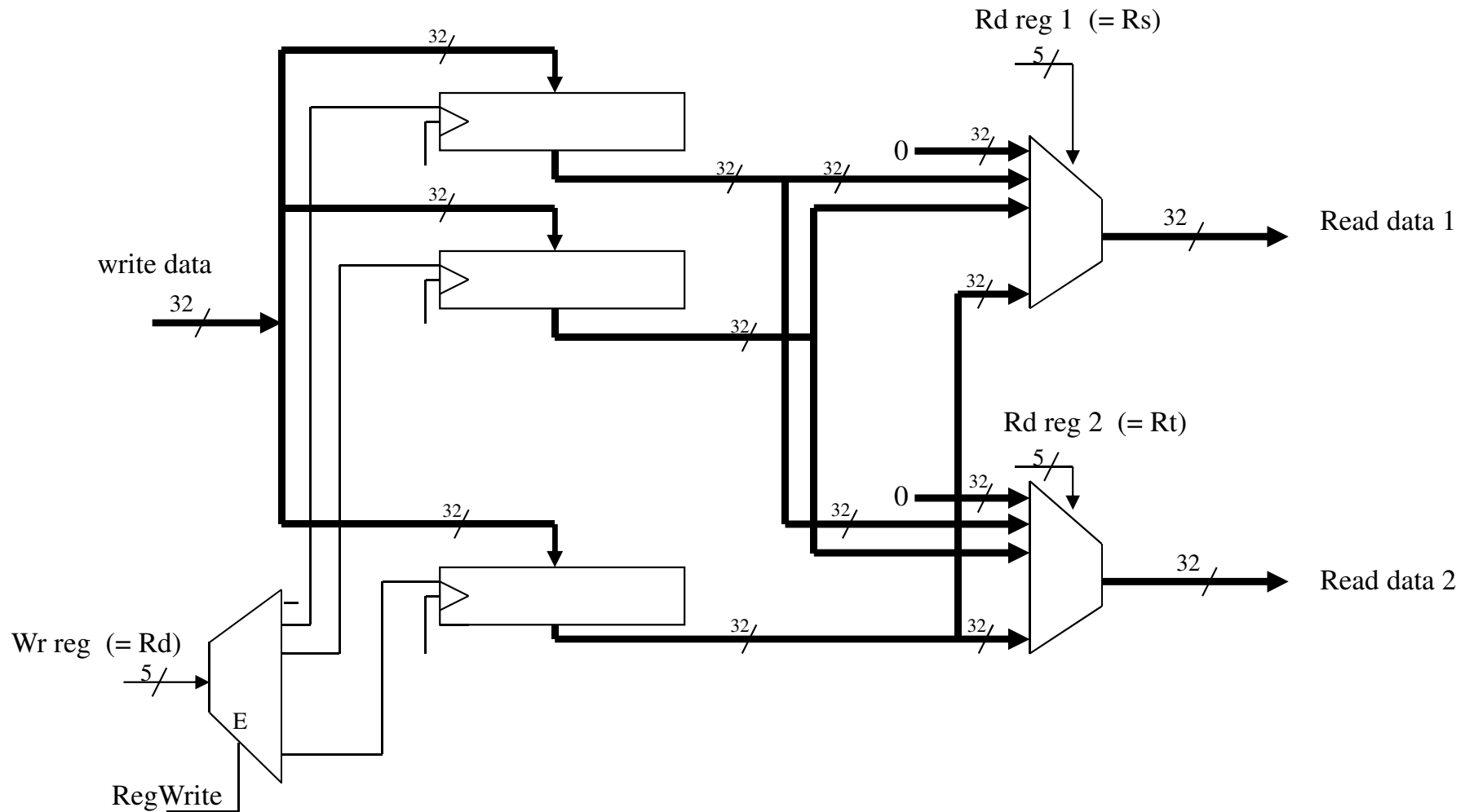
## One possible structure of the Register File





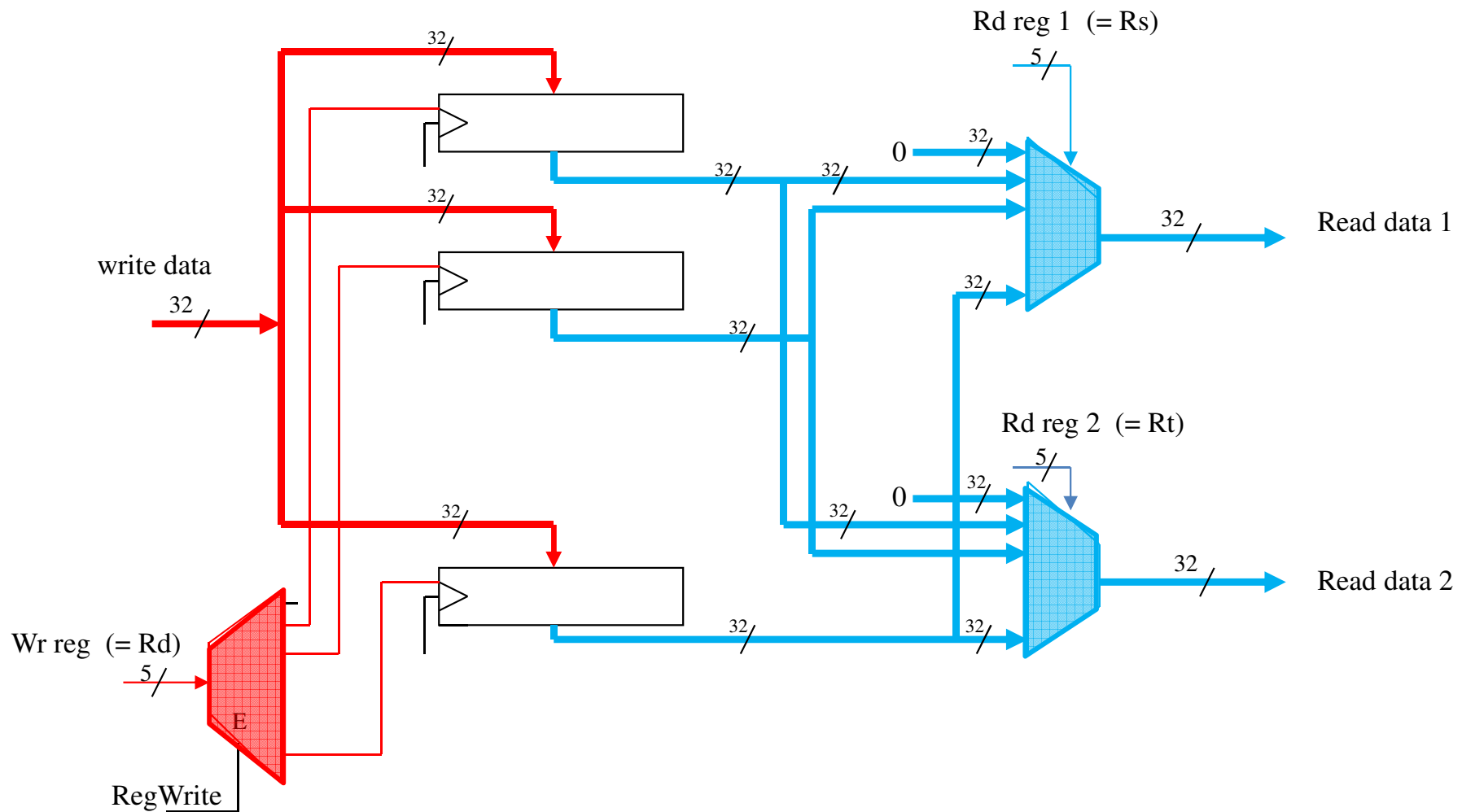
# One possible structure of the Register File



# Dual port async read memory - I

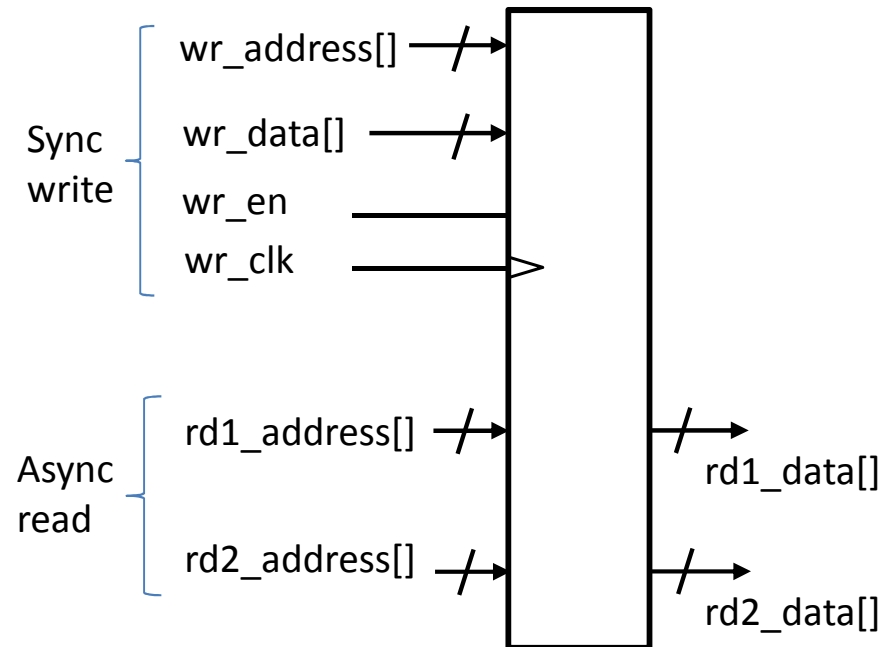

Data will be written to this memory on the rising edge of `wr_clk` if `wr_en` is '1'  
In that case the `wr_data` will be written into `wr_address` in the memory

Data can be read at all times (async read) from `rd1_address`. It appears at `rd1_data` output.

An additional read can be done at the same time (also async read) from `rd2_address`.  
That data appears at the `rd2_data` output.

**You get a `single_port_memory.vhd` file and a `dual_port_memory.empty` file and need to convert the single port memory to a dual port one.**

# Dual port async read memory - II


```

library ieee;
use ieee.std_logic_1164.all;
use ieee.std_logic_arith.all;

entity dual_port_memory_no_CLK_read is
  GENERIC(
    width : integer :=32;
    depth : integer :=32 );

  port (
    wr_address  : in  INTEGER range depth-1 downto 0;
    wr_data     : in  STD_LOGIC_VECTOR(width-1 downto 0);
    wr_clk      : in  STD_LOGIC;
    wr_en       : in  STD_LOGIC;
    --
    rd1_address : in  integer range depth-1 downto 0;
    rd1_data    : out std_logic_vector(width-1 downto 0);
    --
    rd2_address : in  integer range depth-1 downto 0;
    rd2_data    : out std_logic_vector(width-1 downto 0) );

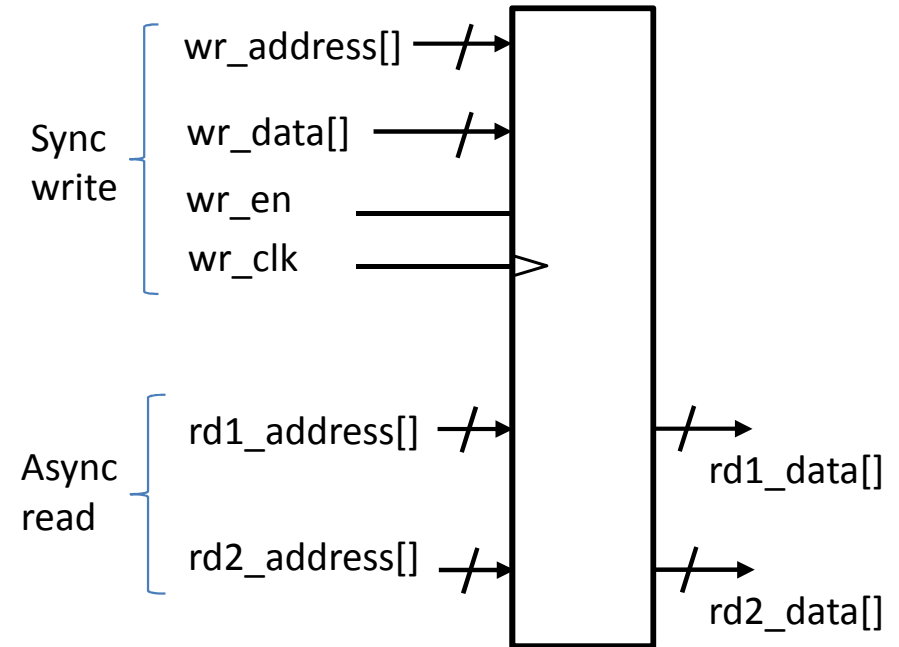end entity dual_port_memory_no_CLK_read;
  
```



In this device we would like to choose the data width (in bits) and the memory depth (in addresses) when we use this device.

For that we use the **GENERIC** statement.

We also give default values

# Dual port async read memory - IV

-- connecting the GPR to the memory

GPR\_file : dual\_port\_memory\_no\_CK\_read

generic map (32, 32)

port map(

wr\_address => conv\_integer(wr\_reg),

wr\_data => GPR\_wr\_data,

wr\_clk => CK,

wr\_en => Reg\_Write,

rd1\_address => conv\_integer(rd\_reg1),

rd1\_data => GPR\_rd\_data1,


rd2\_address => conv\_integer(rd\_reg2),

rd2\_data => GPR\_rd\_data2


);

The General Purpose  
Register file we build has  
32 addresses of 32 bits  
each (width=32,  
depth=32).

 Note that the addresses we  
connect to the memory are  
converted from  
STD\_LOGIC\_VECTORs to  
INTEGERs



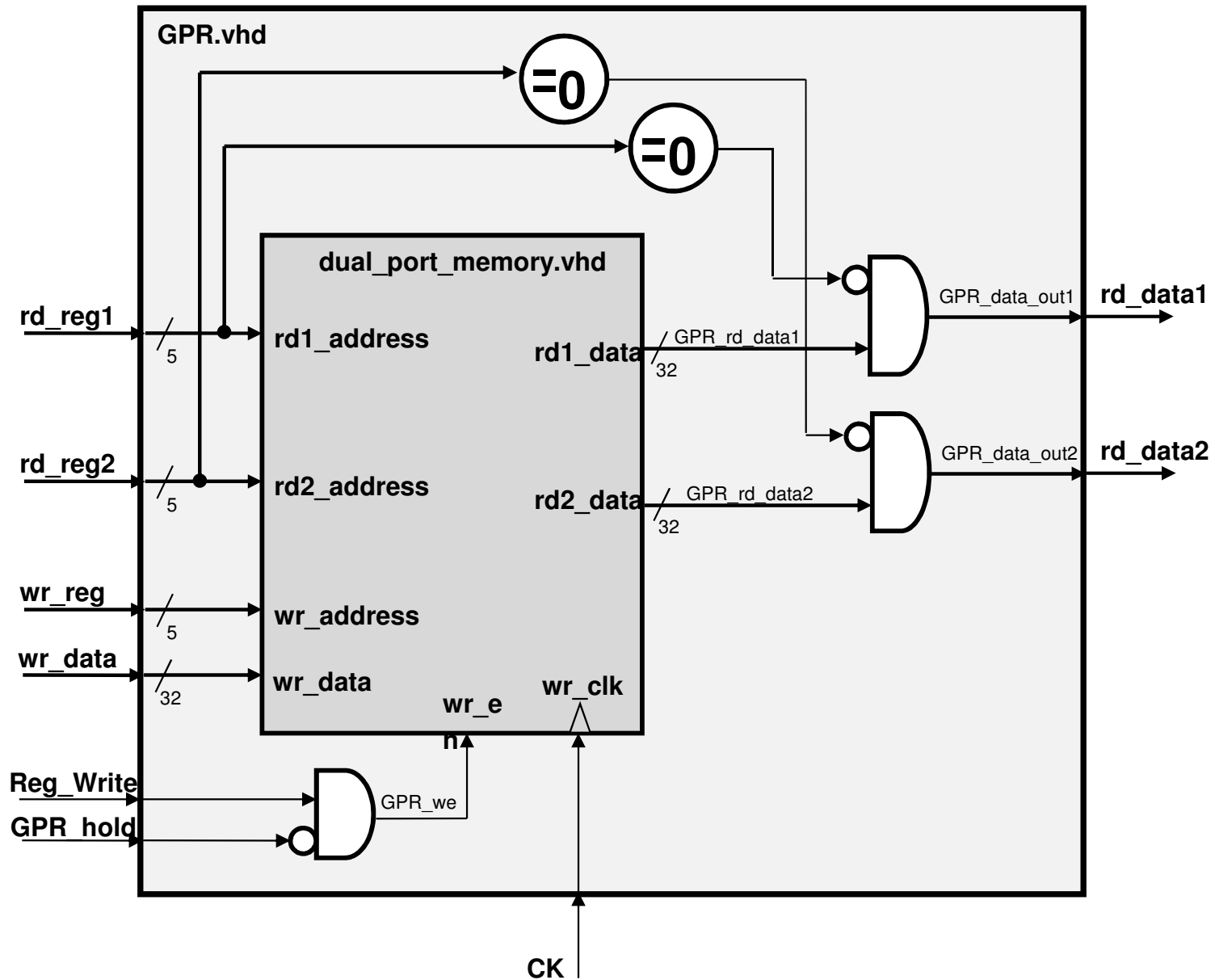**You get GPR.empty file and need to complete the design including making sure  
That register #0 will always read the value 0.**




$$Y = A \cdot \text{sel} + B \cdot \overline{\text{sel}} \quad \text{if A is '0'-s, it becomes } Y = B \cdot \overline{\text{sel}}$$

**The following VHDL code:**

```
process (A, B, sel)
begin
    if sel='1' then
        Y <= A;
    else
        Y <= B;
    end if;
end process;
```

**creates a 2→1 mux:**

 


$$Y = A \cdot \text{sel} + B \cdot \overline{\text{sel}}$$

**The following VHDL code:**

```
process (A, B, sel)
begin
    if sel='1' then
        Y <= A;
    end if;
end process;
```

**creates a latch:**

 

**Since in VHDL the output of a process stays unchanged in cases we do not specify in the “IF”**

**Now it is your turn!**

**Thanks for  
listening!**